

# Karadeniz Technical University

## Faculty of Engineering

Dept. of Comp. Engineering

BİL 107 Final Exam

1. Convert  $0.5625_{10}$  to **single precision floating point** format (**IEEE754**) and represent in **hexadecimal** form.
2. Construct the truth table of a divider circuit to **divide 4 bit unsigned integers** by **2** and output **integer** part of the **quotient**. Use a **Karnaugh** map to produce the simplest **Sum Of Products (SOP)** expression of the circuit. Do **NOT** draw the circuit of minimum **SOP** expression. Use  $x_i$  and  $y_i$  for input and output values respectively.
3. The waveforms shown below are applied on the inputs of a **gated D latch**. Determine and draw the **Q** output waveform if the latch is initially **RESET**.

